

# HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY



*Faculty of Electronics and Electrical Engineering*

## *Lab Report*

### **EMBEDDED SYSTEM**

*Group: 15*

*Class: TT01*

#### *Digital Filters with MATLAB*

*Instructor:*

Bùi Quốc Bảo

**HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY**

<i>Student's names</i>	<i>Student's IDs</i>
Bùi Trung Kiên	2151106
Trần Văn Sỹ	2151251
Nguyễn Thế Khang Hi	2151070

*Academic Year*


*2023 - 2024*

Block Diagram:

### Hardware Selection:

- TP4056 chip
- Battery case for 18650 Lithium Battery
- Plastic cover for the charger

Schematic:

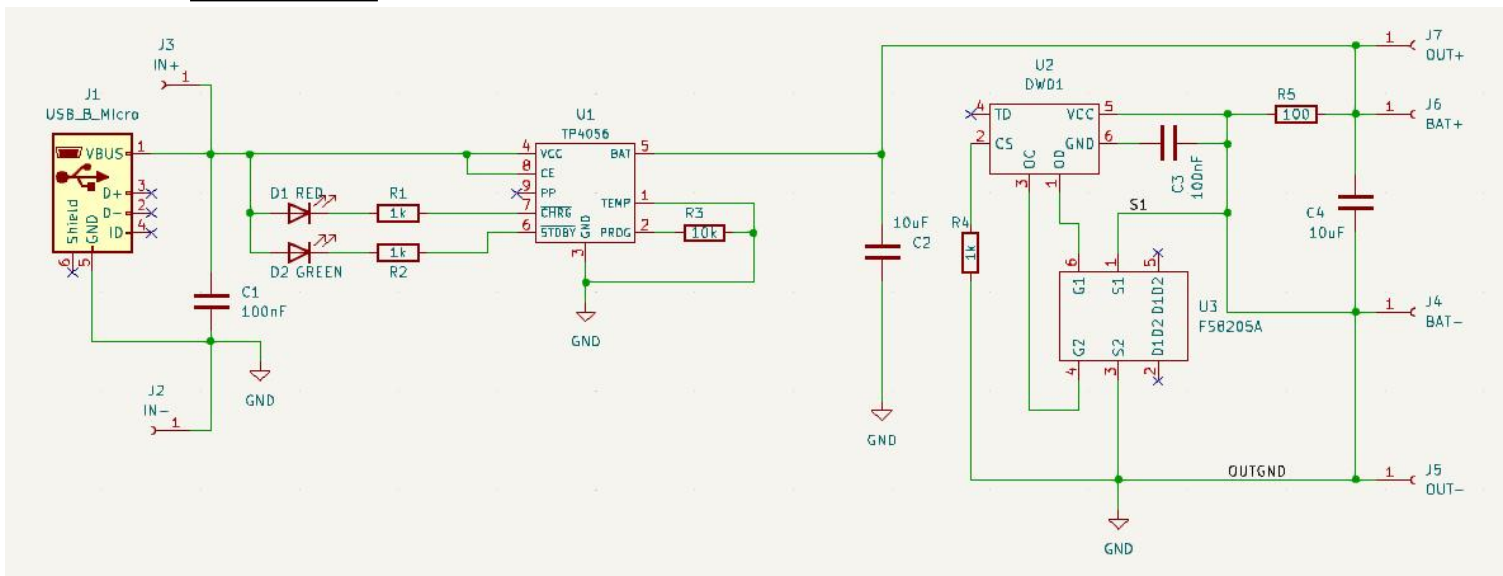

Schematic Explanation:

- TP4056 is the main chip responsible for the charging of the battery, powered by 5V input voltage, supplying charging voltage at 4V and 1A current.
- DW01A is a battery protection IC, responsible for protecting the battery from overcharge
- There is 2 main way of supplying power, either using the 5V USB or using the IN+ and IN- terminals
- RED LED to show if the battery is charging
- GREEN LED to show if the battery is fully charged